

Katwa College
Internal Examination 2022
SEM-VI H
Sub: Physics
Paper: DSE 3

Nuclear and Particle Physics

Full Marks: 10

Time: 30 min

Answer any 5 questions:

5x2=10

1. Design NOR gate using NAND gate.
2. Write the expression of the logic circuit below.